 


4-bit Carry Adder



Name: David (王琮文)
Class: Digital Design with FPGA
Date: Nov. 03, 2025



4-bit Carry Adder

1. Fundamentals

Start with gate-level building blocks and compare RCA and CLA performance.

2. Toolchain

Install and practice with Quartus Prime Lite and ModelSim to run examples.

3. Coding & verification

Implement designs in VHDL and verify them with testbenches in simulation.

4. Hardware & validation

Program the DE2-115 board and validate that hardware behaviour matches ModelSim.

Step 2. Simulation

- half adders
- full adders
- ripple-carry adder (RCA)
- carry-lookahead adder (CLA)

Step 1. Concepts

- Install Quartus Prime
- Install ModelSim
- Write VHDL scripts
- Implement RCA and CLA
- Develop block designs
- Write Testbench
- Simulate in ModelSim

- Design 7-seg display
- Program DE2-115
- Compare simulation and experiments

Step 3. Experiments

Roadmap


Fundamentals

Adder Types

- half adder
- full adder
- ripple-carry adder (RCA)
- carry-lookahead adder (CLA)

Half Adder

- A half adder is a digital circuit that adds two single binary digits (bits) and produces a two-bit sum: a sum bit and a carry bit.
- Logic Gates: one XOR gate (for the sum) and one AND gate (for the carry).
- Sum (S): The result of an XOR gate
 $S = A \oplus B$
- Carry (C): The result of an AND gate
 $C = A \cdot B$
- A key limitation is that it cannot account for a carry-in bit from a previous addition, which is handled by a full adder.

 

Truth Table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full Adder



- A full adder is a digital circuit that adds three single-bit binary numbers and produces a two-bit output: a sum and a carry-out.

- Sum


$$S = A \oplus B \oplus C_{in}$$

- Carry-out
  
$$C = AB + AC_{in} + BC_{in}$$
$$= AB + C_{in} (A \oplus B)$$




Ripple-Carry Adder (RCA)

 

- A ripple-carry adder is a digital circuit that adds two binary numbers by **cascading** multiple **full adder** circuits.
- The carry-out of the first full adder is connected to the carry-in of the second, and so on. The carry "ripples" from the least significant bit to the most significant bit.
- **Propagation delay**: Each full adder must wait for the carry-in from the previous stage, so a significant propagation delay increases with the number of bits.

Carry-Lookahead Adder (CLA)

 

- A CLA uses separate logic to calculate carries in advance. It does this by creating two signals (G and P) for each bit.
- Generate G : A carry is generated if both input bits are one ($G_i = A_i \cdot B_i$).
- Propagate P : A carry is propagated if at least one of the input bits is one and the carry-in is one ($P_i = A_i \oplus B_i$).
- Benefits: much faster carry determination for wide adders; useful in high-speed ALUs and CPUs.
- **Trade-offs:** more hardware (extra gates/wires) and more complex wiring compared with simple ripple-carry adders.

Carry-Lookahead Adder (CLA)

Example: Assume inputs are
 $A = 1011$, $B = 0110$, $C_{in} = 0$.

- $A = a_3a_2a_1a_0 = 1011$

- $B = b_3b_2b_1b_0 = 0110$


- Compute g_i and p_i for each bit:

- $g_0 = a_0 \cdot b_0 = 1 \cdot 0 = 0$, $p_0 = a_0 \oplus b_0 = 1 \oplus 0 = 1$

- $g_1 = 1 \cdot 1 = 1$, $p_1 = 1 \oplus 1 = 0$

- $g_2 = 0 \cdot 1 = 0$, $p_2 = 0 \oplus 1 = 1$

 - $g_3 = 1 \cdot 0 = 0$, $p_3 = 1 \oplus 0 = 1$



- Compute carries using CLA formulas with $c_0 = 0$:

- $c_1 = g_0 + p_0 \cdot c_0 = 0 + 1 \cdot 0 = 0$

- $c_2 = g_1 + p_1g_0 + p_1p_0c_0 = 1 + 0 \cdot 0 + 0 \cdot 1 \cdot 0 = 1$

- $c_3 = g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0 = 0 + 1 \cdot 1 + 1 \cdot 0 \cdot 0 + 1 \cdot 0 \cdot 1 \cdot 0 = 1$

- $c_4 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0 = 0 + 1 \cdot 0 + 1 \cdot 1 \cdot 1 + \dots = 1$

- Compute sums:

- $s_0 = p_0 \oplus c_0 = 1 \oplus 0 = 1$

- $s_1 = p_1 \oplus c_1 = 0 \oplus 0 = 0$

- $s_2 = p_2 \oplus c_2 = 1 \oplus 1 = 0$

- $s_3 = p_3 \oplus c_3 = 1 \oplus 1 = 0$


- Sum bits $s_3s_2s_1s_0 = 0001$ with final carry $c_4 = 1$, so the full result is 1 0001 (binary) = 17 (decimal). The CLA produced carries and sums using the generate/propagate logic rather than waiting bit-by-bit propagation

Toolchain

Installation & Practice

- Quartus Prime Lite
- ModelSim
- VHDL Coding
- Block Design

Install Quartus Prime Lite

 

The screenshot shows the Intel FPGA Software Download Center interface. At the top, there is the Intel logo, a user profile icon, a globe icon, and a search icon. Below the header, the text "FPGA Software Download Center" is displayed with a dropdown arrow. The main content area has a dark blue background with white text. The title "Intel® Quartus® Prime Lite Edition Design Software Version 24.1 for Linux" is prominently displayed. Below the title, there is a table-like structure with the following details:

ID	849769
Date	3/17/2025
Software Type	FPGA Development Tools
Software Package	Quartus® Prime Lite
Version	24.1
Operating Systems	Linux

- Source

<https://www.intel.com/content/www/us/en/software-kit/849769/intel-quartus-prime-lite-edition-design-software-version-24-1-for-linux.html>

Install ModelSim



The screenshot shows the Intel FPGA Software Download Center interface. At the top, the Intel logo is on the left, and user, globe, and search icons are on the right. Below the logo is the text 'FPGA Software Download Center' with a dropdown arrow. The main heading is 'ModelSim-Intel® FPGAs Standard Edition Software Version 20.1'. Below this, there are five rows of information, each with a label and a value in a white box with a dropdown arrow:

ID	750637
Date	9/14/2020
Software Type	Simulation Tools
Software Package	ModelSim-Intel® FPGAs Standard
Version	20.1
Operating Systems	Windows, Linux

- Source

<https://www.intel.com/content/www/us/en/software-kit/750637/modelsim-intel-fpgas-standard-edition-software-version-20-1.html>

VHDL Basics

- VHDL, which stands for **Very High-Speed Integrated Circuit Hardware Description Language**, is a programming language used to describe the behavior and structure of digital electronic circuits. It allows engineers to model, simulate, and synthesize digital systems, from simple logic gates to complex integrated circuits, for use in applications like FPGAs and ASICs. VHDL handles both concurrent and sequential operations and incorporates timing specifications, and it is standardized by the IEEE.
- NandLand Tutorial – Introduction to VHDL
 - <https://nandland.com/introduction-to-vhdl-for-beginners-with-code-examples/>

Design Entry in Quartus

The desired circuit is specified either by means of a **schematic diagram**, or by using a **hardware description language**, such as Verilog or VHDL.

 



Figure 1. Typical CAD flow.

Coding & Verification

Simulation

- Implement full adders with VHDL
 - Implement ripple-carry adder (RCA) with VHDL
 - Implement carry-lookahead adder (CLA) with VHDL
 - Develop schematic designs with I/O constraints
 - Write and compile testbenches on ModelSim
-


Implement a full adder with VHDL

 

```
7  entity full_adder is
8      port (
9          a  : in  std_logic;
10         b  : in  std_logic;
11         cin : in  std_logic;
12         s   : out std_logic;
13         cout: out std_logic
14     );
15 end entity;
16
17 architecture rtl of full_adder is
18 begin
19     s    <= a xor b xor cin;
20     cout <= (a and b) or (a and cin) or (b and cin);
21 end architecture;
```


Implement an RCA with VHDL

ripple-carry adder (RCA) = 4 full adders

 


```
8  entity rca_4bit is
9      port(
10         a      : in  std_logic_vector(3 downto 0);
11         b      : in  std_logic_vector(3 downto 0);
12         cin    : in  std_logic;
13         sum    : out std_logic_vector(3 downto 0);
14         cout   : out std_logic
15     );
16 end entity;

17
18 architecture structural of rca_4bit is
19     signal c : std_logic_vector(4 downto 0);
20 begin
21     c(0) <= cin;
22
23     fa0: entity work.full_adder(rtl)
24         port map(a(0), b(0), c(0), sum(0), c(1));
25
26     fa1: entity work.full_adder(rtl)
27         port map(a(1), b(1), c(1), sum(1), c(2));
28
29     fa2: entity work.full_adder(rtl)
30         port map(a(2), b(2), c(2), sum(2), c(3));
31
32     fa3: entity work.full_adder(rtl)
33         port map(a(3), b(3), c(3), sum(3), c(4));
34
35     cout <= c(4);
36 end architecture;
```

Implement an CLA with VHDL

carry-lookahead adder (CLA)

 

```

25 architecture rtl of cla_4bit is
26     -- propagate and generate for each bit:
27     -- p(i) = a(i) xor b(i) -> indicates this bit will propagate an incoming carry
28     -- g(i) = a(i) and b(i) -> indicates this bit will generate a carry regardless of incoming carry
29     signal p, g : std_logic_vector(3 downto 0);
30
31     -- carries: c(0) is input carry (cin), c(4) is output carry (cout)
32     signal c : std_logic_vector(4 downto 0);
33 begin
34     -- assign initial carry
35     c(0) <= cin;
36
37     -- generate p and g for each bit 0..3
38     gen_pg: for i in 0 to 3 generate
39         p(i) <= a(i) xor b(i);    -- propagate
40         g(i) <= a(i) and b(i);    -- generate
41     end generate gen_pg;
42
43     -- carry equations expanded (lookahead expansion for clarity)
44     -- c(1) is carry into bit 1 (i.e., carry out from bit 0)
45     c(1) <= g(0) or (p(0) and c(0));
46
47     -- c(2) is carry into bit 2 (carry out from bit 1)
48     c(2) <= g(1) or (p(1) and g(0)) or (p(1) and p(0) and c(0));
49
50     -- c(3) is carry into bit 3 (carry out from bit 2)
51     c(3) <= g(2) or (p(2) and g(1)) or (p(2) and p(1) and g(0)) or (p(2) and p(1) and p(0) and c(0));
52
53     -- c(4) is final carry out (carry out from bit 3)
54     c(4) <= g(3)
55         or (p(3) and g(2))
56         or (p(3) and p(2) and g(1))
57         or (p(3) and p(2) and p(1) and g(0))
58         or (p(3) and p(2) and p(1) and p(0) and c(0));
59
60     -- sum bits: sum(i) = p(i) xor c(i) (where c(i) is carry into bit i)
61     sum(0) <= p(0) xor c(0);
62     sum(1) <= p(1) xor c(1);
63     sum(2) <= p(2) xor c(2);
64     sum(3) <= p(3) xor c(3);
65
66     -- final carry out
67     cout <= c(4);
68
69 end rtl;


```

Test Cases

- Test Case #1: enabled, $3 + 5 \rightarrow$ ideal sum = 8
- Test Case #2: enabled, $7 + 9 \rightarrow$ ideal carry-out will be one
- Test Case #3: enabled, $5 + 2 \rightarrow$ ideal sum = 7
- Test Case #4: disabled, $1 + 1 \rightarrow$ outputs = previous value (sum = 7)
- Test Case #5: enabled, $15 + 2 \rightarrow$ (sum, cout) = (1, 1)
- Test Case #6: enabled, $2 + 4 \rightarrow$ ideal sum = 6

Start compilation and see RTL simulation

ModelSim®

 

Hardware & Validation

Experiments with DE2-115

- 7-Segment Display
 - Block Designs
 - I/O Pins
 - DE2-115 Programming
-

Altera DE2-115

The Altera DE2-115 is an FPGA development and education kit that features the Cyclone IV EP4CE115 FPGA, which offers 114,480 logic elements (LEs), up to 3.9 Mbits of RAM, and 266 multipliers.



DE2-115




(幣別: 台幣)

\$28,630

學術價: \$15,545



Altera DE2-115 教育開發平台

altera™

 

7-Segment Display

  A 7-segment display consists of seven LEDs arranged in a figure-eight pattern. Each segment is labeled A through G, and when illuminated in specific combinations, they form digits (0–9) and letters (A–F).




7-Segment Display on DE2-115

```

58 with digit select
59   seg_pat <=
60     "0000001" when "0000", -- 0: a b c d e f ON, g OFF
61     "1001111" when "0001", -- 1
62     "0010010" when "0010", -- 2
63     "0000110" when "0011", -- 3
64     "1001100" when "0100", -- 4
65     "0100100" when "0101", -- 5
66     "0100000" when "0110", -- 6
67     "0001111" when "0111", -- 7
68     "0000000" when "1000", -- 8: all segments ON
69     "0000100" when "1001", -- 9
70     "0000001" when "1010", -- 10 -> same pattern as 0 (adjust if you want 'A')
71     "1001111" when "1011", -- 11 -> same as 1
72     "0010010" when "1100", -- 12 -> same as 2
73     "0000110" when "1101", -- 13 -> same as 3
74     "1001100" when "1110", -- 14 -> same as 4
75     "0100100" when "1111", -- 15 -> same as 5
76     "1111111" when others; -- default: all segments OFF (blank)

```


Digit	Display	Input	A	B	C	D	E	F	G
0	0	0000	on	on	on	on	on	on	off
1	1	0001	off	on	on	off	off	off	off
2	2	0010	on	on	off	on	on	off	on
3	3	0011	on	on	on	on	off	off	on
4	4	0100	off	on	on	off	off	on	on
5	5	0101	on	off	on	on	off	on	on
6	6	0110	on	off	on	on	on	on	on
7	7	0111	on	on	on	off	off	off	off
8	8	0111	on	on	on	on	on	on	on
9	9	1001	on	on	on	on	off	on	on

 

Display CLA Results on DE2-115


(CLA = carry-lookahead adder)

Assume `rst_n = '1'` and `en = '1'`.

 


[Output Case] (decimal) summation of 2 numbers	(binary) sum in VHDL	7-segment display	carry-out in VHDL	LED status
6	0110	06	0	OFF
8	1000	08	0	OFF
10	1010	10	0	OFF
15	1111	15	0	OFF
16	0000	00	1	ON
17	0001	01	1	ON

Block Design

 

Block Design: I/O Pins

 

Pin Assignment to DE2-115

Check the user manual and refer to the pins like SW[•], LEDR[•], and HEX1[•] for switches, LEDs, and 7-segment displays, respectively.

Table 4-1 Pin Assignments for Slide Switches

Signal Name	FPGA Pin No.	Description	I/O Standard
SW[0]	PIN_AB28	Slide Switch[0]	Depending on JP7
SW[1]	PIN_AC28	Slide Switch[1]	Depending on JP7
SW[2]	PIN_AC27	Slide Switch[2]	Depending on JP7
SW[3]	PIN_AD27	Slide Switch[3]	Depending on JP7

Table 4-3 Pin Assignments for LEDs

Signal Name	FPGA Pin No.	Description	I/O Standard
LEDR[0]	PIN_G19	LED Red[0]	2.5V
LEDR[1]	PIN_F19	LED Red[1]	2.5V
LEDR[2]	PIN_E19	LED Red[2]	2.5V

Table 4-4 Pin Assignments for 7-segment Displays

Signal Name	FPGA Pin No.	Description	I/O Standard
HEX0[0]	PIN_G18	Seven Segment Digit 0[0]	2.5V
HEX0[1]	PIN_F22	Seven Segment Digit 0[1]	2.5V
HEX0[2]	PIN_E17	Seven Segment Digit 0[2]	2.5V

	Status	From	To	Assignment Name	Value	Enabled	Entity
1	✓ Ok		in clk	Location	PIN_Y2	Yes	
2	✓ Ok		in clk	I/O Standard	3.3-V LVTTL	Yes	ripple_...display
3	✓ Ok		in rst_n	Location	PIN_AC25	Yes	
4	✓ Ok		in a[0]	Location	PIN_AB28	Yes	
5	✓ Ok		in a[1]	Location	PIN_AC28	Yes	
6	✓ Ok		in a[2]	Location	PIN_AC27	Yes	
7	✓ Ok		in a[3]	Location	PIN_AD27	Yes	
8	✓ Ok		in b[0]	Location	PIN_AB27	Yes	
9	✓ Ok		in b[1]	Location	PIN_AC26	Yes	
10	✓ Ok		in b[2]	Location	PIN_AD26	Yes	
11	✓ Ok		in b[3]	Location	PIN_AB26	Yes	
12	✓ Ok		in en	Location	PIN_AB25	Yes	
13	✓ Ok		out carry	Location	PIN_G19	Yes	
14	✓ Ok		out hex0_a	Location	PIN_M24	Yes	
15	✓ Ok		out hex0_b	Location	PIN_Y22	Yes	
16	✓ Ok		out hex0_c	Location	PIN_W21	Yes	
17	✓ Ok		out hex0_d	Location	PIN_W22	Yes	
18	✓ Ok		out hex0_e	Location	PIN_W25	Yes	
19	✓ Ok		out hex0_f	Location	PIN_U23	Yes	
20	✓ Ok		out hex0_g	Location	PIN_U24	Yes	
21	✓ Ok		out hex0_a	I/O Standard	3.3-V LVTTL	Yes	ripple_...display
22	✓ Ok		out hex0_b	I/O Standard	3.3-V LVTTL	Yes	ripple_...display
23	✓ Ok		out hex0_c	I/O Standard	3.3-V LVTTL	Yes	ripple_...display
24	✓ Ok		out hex0_d	I/O Standard	3.3-V LVTTL	Yes	ripple_...display
25	✓ Ok		out hex0_e	I/O Standard	3.3-V LVTTL	Yes	ripple_...display

User Manual:

https://www.terasic.com.tw/attachment/archive/502/DE2_115_User_manual.pdf

After compilation ...

Tasks	Compilation
Task	
✓	▶ Compile Design
✓	▶ ▶ Analysis & Synthesis
✓	▶ ▶ Fitter (Place & Route)
✓	▶ ▶ Assembler (Generate programming files)
✓	▶ ▶ Timing Analysis
✓	▶ ▶ EDA Netlist Writer
	Edit Settings
	Program Device (Open Programmer)

carry-lookahead adder (CLA)

Flow Summary	
<<Filter>>	
Flow Status	Successful - Sat Nov 15 22:10:51 2025
Quartus Prime Version	24.1std.0 Build 1077 03/04/2025 SC Lite Edition
Revision Name	top_level
Top-level Entity Name	ripple_adder_display
Family	Cyclone IV E
Device	EP4CE115F29C7
Timing Models	Final
Total logic elements	28 / 114,480 (< 1 %)
Total registers	5
Total pins	26 / 529 (5 %)
Total virtual pins	0
Total memory bits	0 / 3,981,312 (0 %)
Embedded Multiplier 9-bit elements	0 / 532 (0 %)
Total PLLs	0 / 4 (0 %)

total logic elements = 28

ripple-carry adder (RCA)

Flow Summary	
<<Filter>>	
Flow Status	Successful - Sat Nov 15 22:22:08 2025
Quartus Prime Version	24.1std.0 Build 1077 03/04/2025 SC Lite Edition
Revision Name	top_level
Top-level Entity Name	ripple_adder_display
Family	Cyclone IV E
Device	EP4CE115F29C7
Timing Models	Final
Total logic elements	21 / 114,480 (< 1 %)
Total registers	5
Total pins	26 / 529 (5 %)
Total virtual pins	0
Total memory bits	0 / 3,981,312 (0 %)
Embedded Multiplier 9-bit elements	0 / 532 (0 %)
Total PLLs	0 / 4 (0 %)

total logic elements = 21

Resource Usage

carry-lookahead adder (CLA)


>

ripple-carry adder (RCA)


Analysis & Synthesis Resource Usage Summary		
 <<Filter>>		
	Resource	Usage
1	Estimated Total logic elements	28
2		
3	Total combinational functions	28
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	19
2	-- 3 input functions	4
3	-- <=2 input functions	5
5		
6	▼ Logic elements by mode	
1	-- normal mode	25
2	-- arithmetic mode	3
7		
8	▼ Total registers	5
1	-- Dedicated logic registers	5
2	-- I/O registers	0
9		
10	I/O pins	26
11		
12	Embedded Multiplier 9-bit elements	0
13		
14	Maximum fan-out node	rst_n~input
15	Maximum fan-out	13
16	Total fan-out	149
17	Average fan-out	1.75

Analysis & Synthesis Resource Usage Summary		
 <<Filter>>		
	Resource	Usage
1	Estimated Total logic elements	21
2		
3	Total combinational functions	21
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	15
2	-- 3 input functions	0
3	-- <=2 input functions	6
5		
6	▼ Logic elements by mode	
1	-- normal mode	18
2	-- arithmetic mode	3
7		
8	▼ Total registers	5
1	-- Dedicated logic registers	5
2	-- I/O registers	0
9		
10	I/O pins	26
11		
12	Embedded Multiplier 9-bit elements	0
13		
14	Maximum fan-out node	rst_n~input
15	Maximum fan-out	8
16	Total fan-out	122
17	Average fan-out	1.56

Start my experiment on Altera DE2-115

 


Experiment: $2 + 4 = 6$

 

$\overline{\text{en}}$ $\text{rst_nb}[3..0]$ $\text{a}[3..0]$


Experiment: disabled.

 The previous value remains even if the inputs change.




en↑

Experiment: $6 + 9 = 15$

 



`en_rst_nb[3..0]` `a[3..0]`

Experiment: $7 + 9 = \text{carry-out}$

 

 Experiment: $15 + 7 = 6 + \text{carry-out}$



 

Experiment Video

4-bit Carry Adder

Conclusion

- ripple-carry adder (RCA)
- carry-lookahead adder (CLA)
- ModelSim & DE2-115

Design trade-offs

Ripple-carry adder (RCA)

- **Strength:** Minimal logic and straightforward implementation make the RCA efficient in resource usage and easy to verify.
- **Limitation:** Carry propagation is sequential, so worst-case propagation delay grows linearly with bit width and becomes the dominant performance bottleneck as operand size increases.

Carry-lookahead adder (CLA)

- **Strength:** Generates carries in parallel using generate/propagate logic, enabling much faster addition for wider bit widths because carry computation can be performed concurrently.
- **Limitation:** Increased complexity and higher utilization of FPGA logic resources; the CLA requires more LUTs and routing, which can complicate timing closure on the target device.

Conclusion

- For small bit widths or resource-constrained designs, the ripple-carry adder (RCA) is a pragmatic, low-overhead choice.
- For high-performance or wide-operand addition where throughput and latency are critical, the carry-lookahead adder (CLA) is preferable despite its larger area and implementation complexity.
- Our combined simulation and hardware results provide consistent evidence supporting these recommendations.

電子與AI應用專業人才養成班第三期

FPGA與數位IC晶片設計

Thanks for your attention



陽明交大雷射系統研究中心